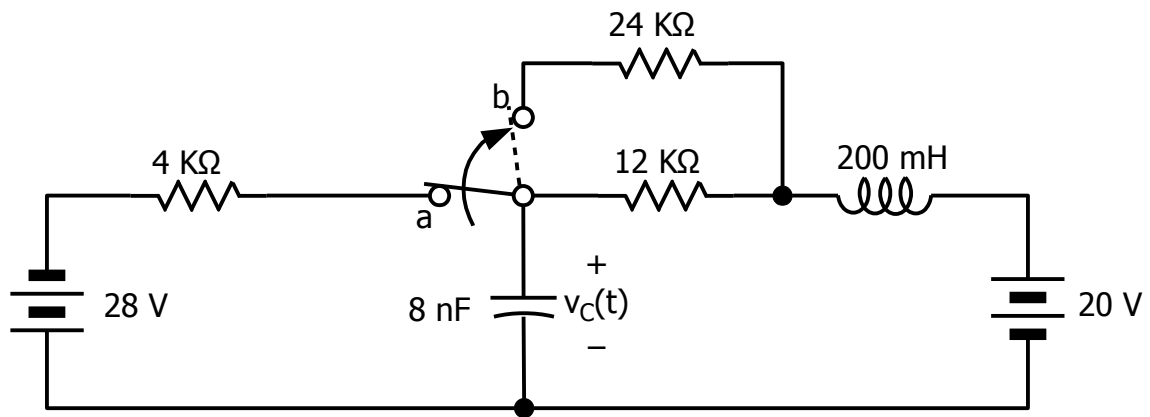


EE3 Fall 2020
Practice Problems 4



1. The switch has been in position a for a long time. All transients have died out. At $t = 0$, the switch moves instantaneously to position b.
 - a. At $t=0^-$ (the last instant that the switch is in position a), what is the current through the capacitor?
 - b. At $t=0^-$ (the last instant that the switch is in position a), what is the voltage across the capacitor? -16 V
 - c. At $t=0^+$ (the first instant that the switch is in position b), the current through the capacitor is the same as in Part a. True False
 - d. At $t=0^+$ (the first instant that the switch is in position b), the voltage across the inductor is the same as at $t=0^-$. True False
 - e. At $t=0^+$ (the first instant that the switch is in position b), what is the voltage across the inductor?


12 V; + at right end

EE3 Fall 2020 Practice Problems 4

2. This is a second-order circuit. There is an initial voltage on the capacitor $v(0^-) = 12$ V, and an initial current in the inductor $i_L(0^-) = 30$ mA. In order to solve the differential equation for $v(t)$, the following values must be found:

- $i_C(0^+)$
- $i_R(0^+)$
- $dv(t)/dt|_{t=0^+}$

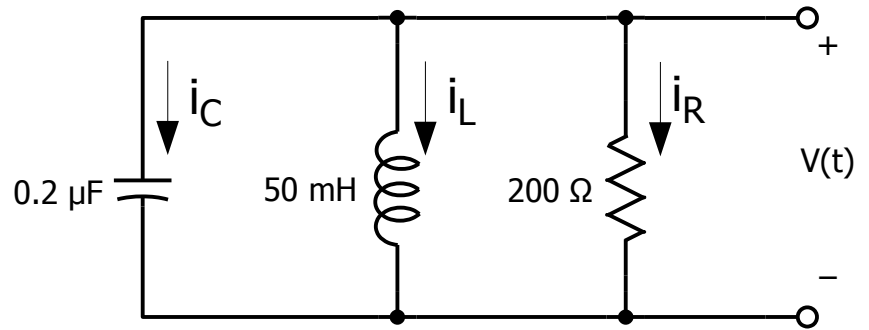Using what you know about inductors, capacitors, and KCL, find these values.




- -90 mA
- 60 mA
- -450 KV/s

EE3 Fall 2020

Practice Problems 4

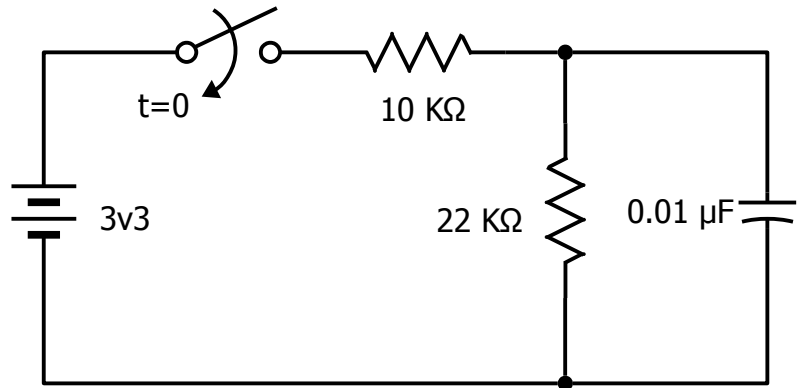- 3a. Find the time constant τ of this circuit. This will require solving the differential equation for the circuit.
- 3b. Then, find only the Thévenin resistance R_{th} of the circuit to the left of the capacitor (consider the capacitor to be the load).
- 3c. Then, compute $R_{th} \cdot C$ and compare to the τ from 3a.



$$\text{Time constant } \tau = 6.875e-5 \text{ s}$$
$$R_{th} \cdot C = 6.875e-5 \text{ s}$$


EE3 Fall 2020

Practice Problems 4

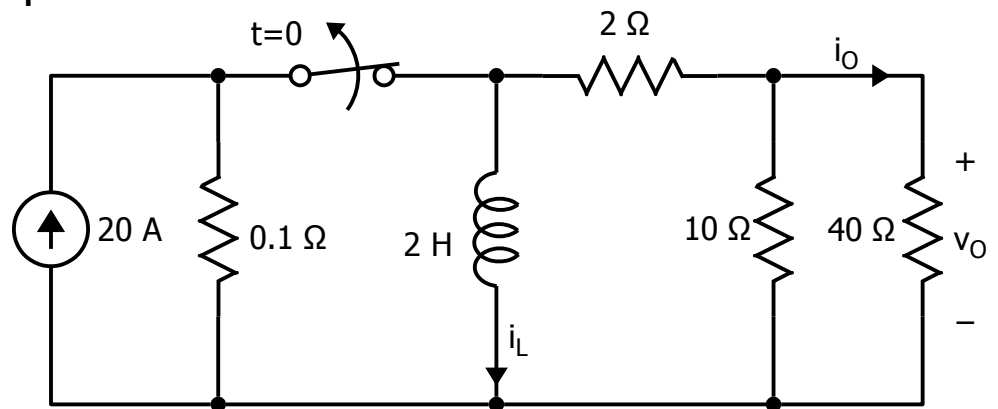4. The switch has been in the position shown for a long time. Find:

- $i_L(0^+)$
- $i_O(0^+)$
- $v_O(0^+)$
- τ for $t=0^+$
- $i_L(0^+)$ for all $t>0$

(HINT: refer to the Lecture 4 video at 22 minutes.)




- $i_L(0^+) = 20 \text{ A}$
- $i_O(0^+) = -4 \text{ A}$
- $v_O(0^+) = -160 \text{ V}$
- $\tau = 0.2 \text{ s}$
- $i_L(t) = 20e^{-5t}$

EE3 Fall 2020

Practice Problems 4

5. The switch has been open for a long time. Find:

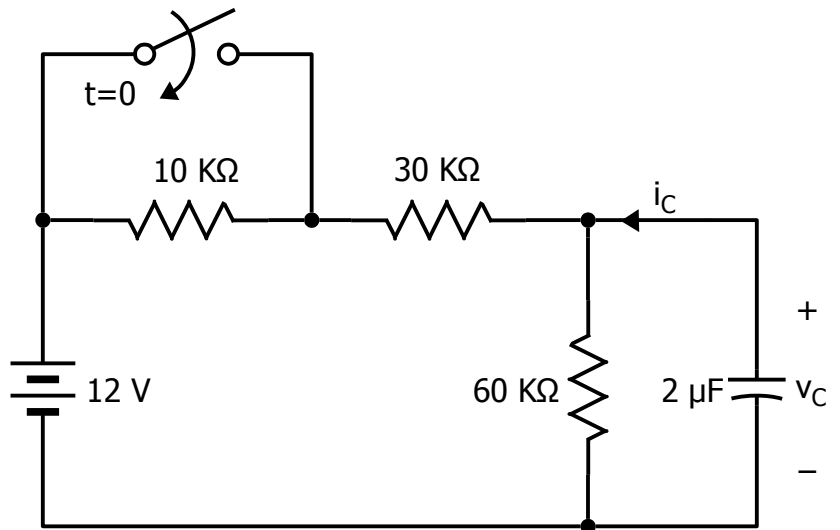- a. $v_C(0^-)$
- b. $v_C(0^+)$
- c. $v_C(\infty)$
- d. $i_C(0^-)$
- e. $i_C(0^+)$



e. 0.04 mA