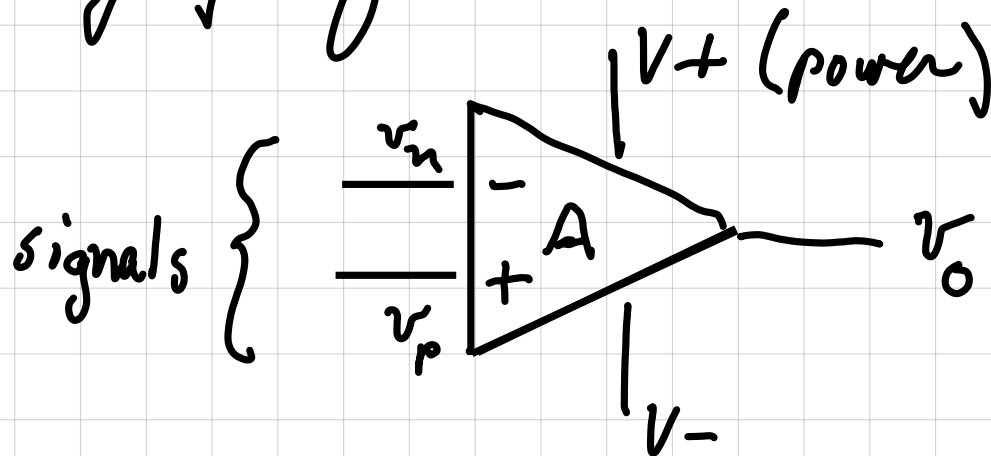


# OPERATIONAL AMPLIFIERS

Highly useful + complex. "Black boxes."





$$v_o = A(v_p - v_n)$$


Characteristics:  $A$  is very large ( $>10^5$ )  
(Design)  $Z_{in}$  is very large ( $\sim 1\text{M}\Omega$ )

$Z_{out}$  is rather small

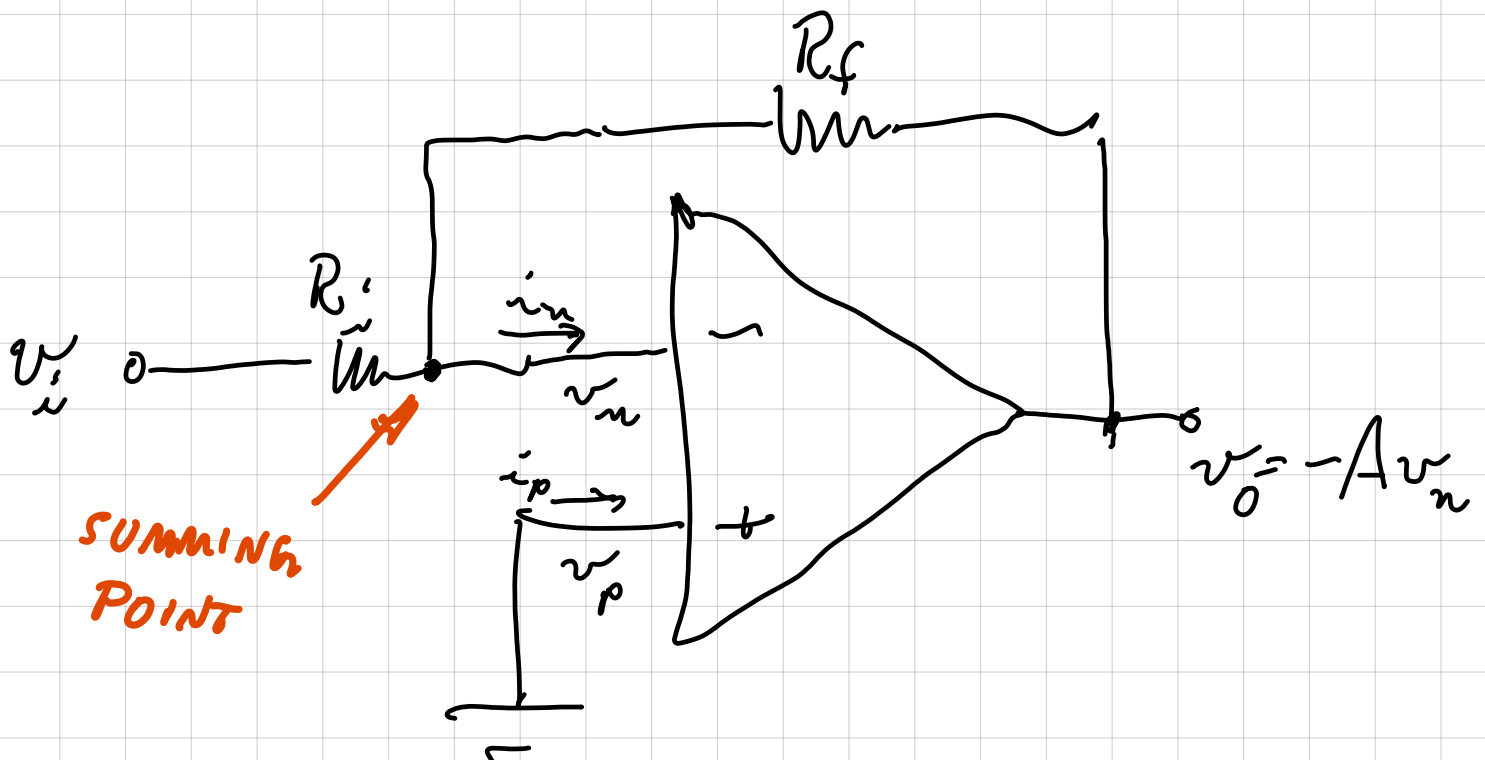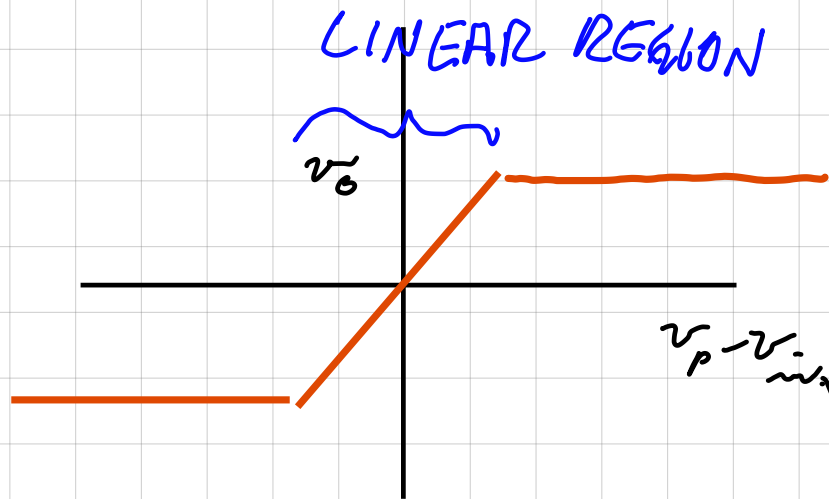move this!  $\left[ \begin{array}{l} \text{"virtual short" betw } v_p \text{ \& } v_n \\ \text{(with nvc feedback).} \end{array} \right.$



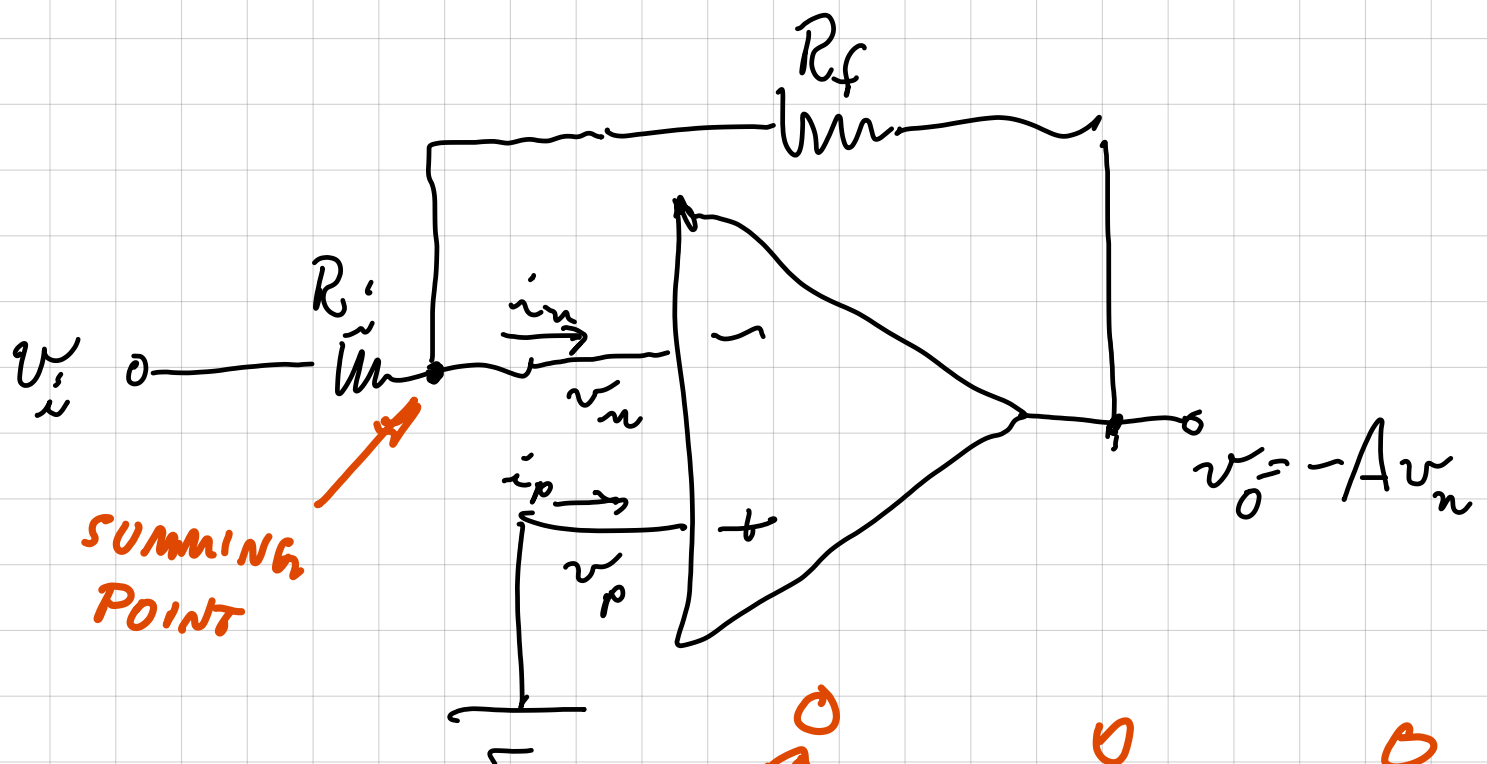Operational Chars: "virtual short"  $v_n = v_p$   
 (summing point ~~constraints~~  $i_n = 0 = i_p$ )




$$v_o = f(v_i, R's) = \frac{v_n - v_o}{R_f} + \frac{v_n - v_i}{R_i} + i_n \approx 0$$

$$v_o = -\frac{R_f}{R_i} v_i \quad [\text{inverting op amp ckt}]$$

Load does not figure into the analysis,

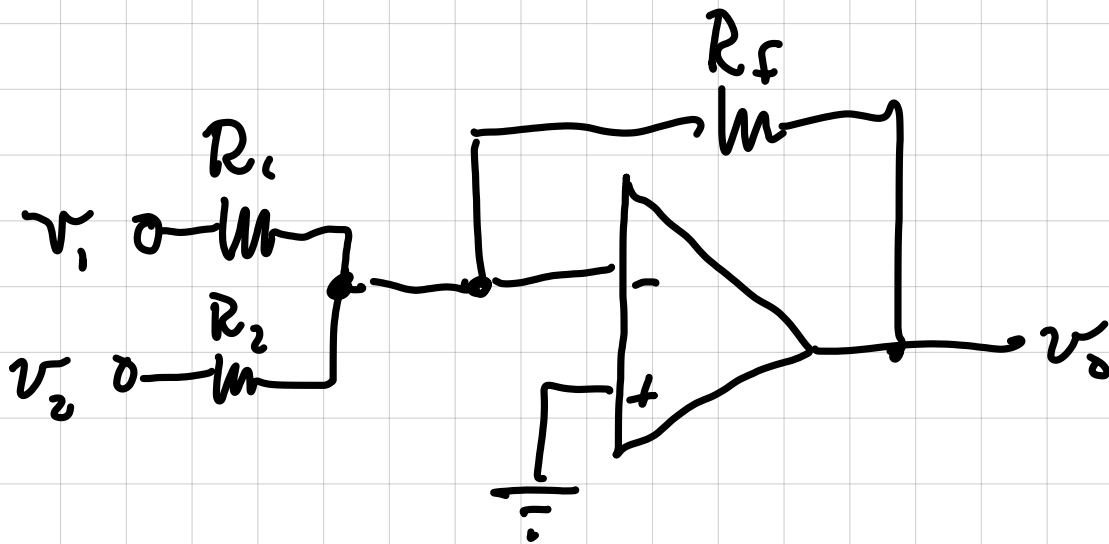cuz  $Z_{out}$  w/ nve fb. is very small.




$$\frac{v_n - v_1}{R_1} + \frac{v_n - v_2}{R_2} + \frac{v_n - v_o}{R_f} = 0$$

$$\frac{v_o}{R_f} = -\left[\frac{v_1}{R_1} + \frac{v_2}{R_2}\right] \Rightarrow v_o = -R_f \left[\frac{v_1}{R_1} + \frac{v_2}{R_2}\right]$$

if  $R_1 = R_2 = R_i$


$$v_o = -\frac{R_f}{R_i} (v_1 + v_2)$$

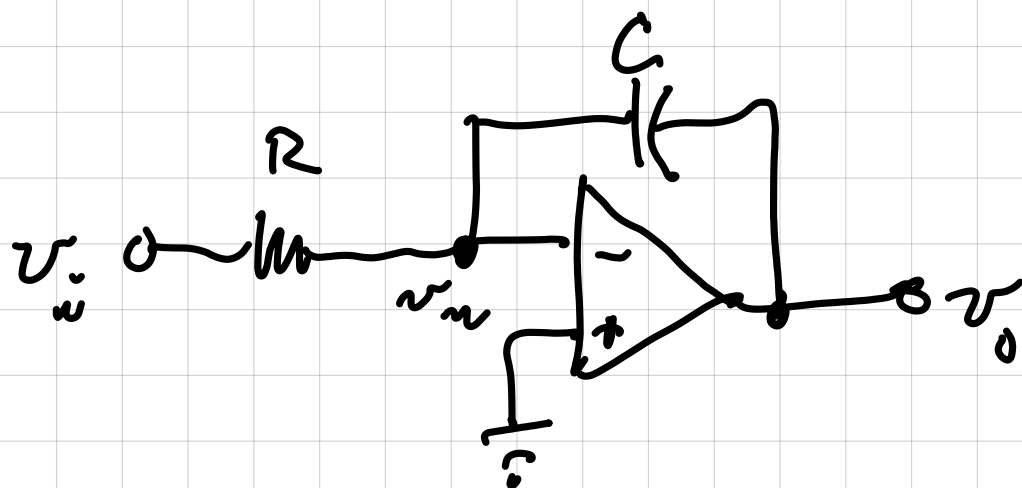

$$\frac{v_n - v_i}{R} + C \frac{d}{dt} (v_n - v_o) = 0$$

$$C \frac{dv_o}{dt} = -\frac{v_i}{R} \Rightarrow \frac{dv_o}{dt} = -\frac{1}{RC} v_i$$

$$v_o = -\frac{1}{RC} \int v_i dt$$

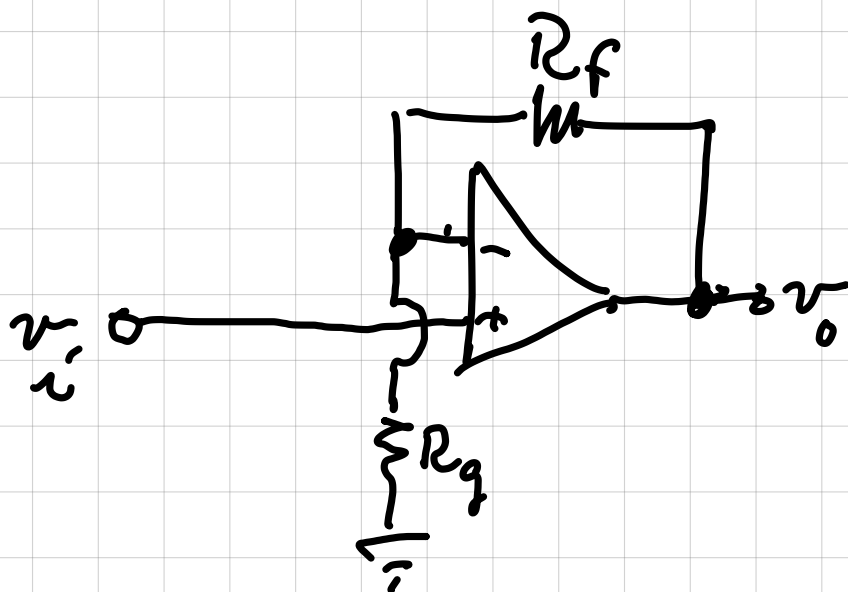


$$\frac{v_n - v_o}{R_f} + \frac{v_n}{R_g} = 0$$

$$v_n = v_i \quad [\text{summing point constraint}]$$


$$\frac{v_i - v_o}{R_f} + \frac{v_i}{R_g} = 0$$
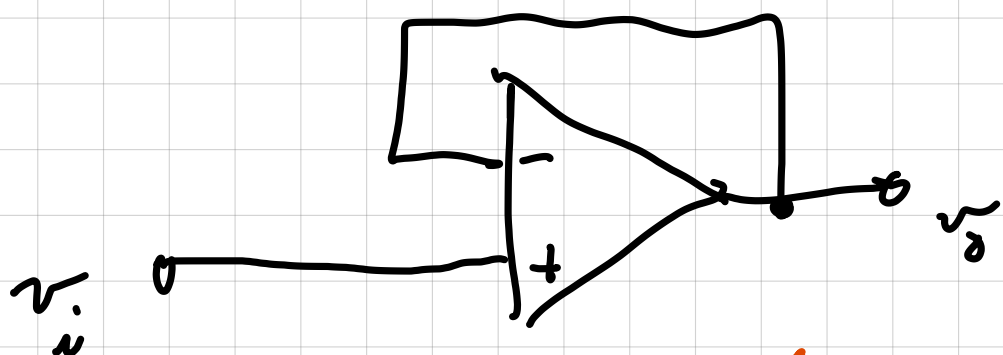
$$\begin{aligned} \frac{v_o}{R_f} &= \frac{v_i}{R_f} + \frac{v_i}{R_g} \Rightarrow v_o = v_i + \frac{R_f v_i}{R_g} = v_i \left( 1 + \frac{R_f}{R_g} \right) \\ &= v_i \left( 1 + \frac{R_f}{R_g} \right) \quad [\text{non-inverting op amp ckt}] \end{aligned}$$



$$v_o = ? = v_i \left( 1 + \frac{R_f}{\frac{R_g}{\infty}} \right) = v_i$$

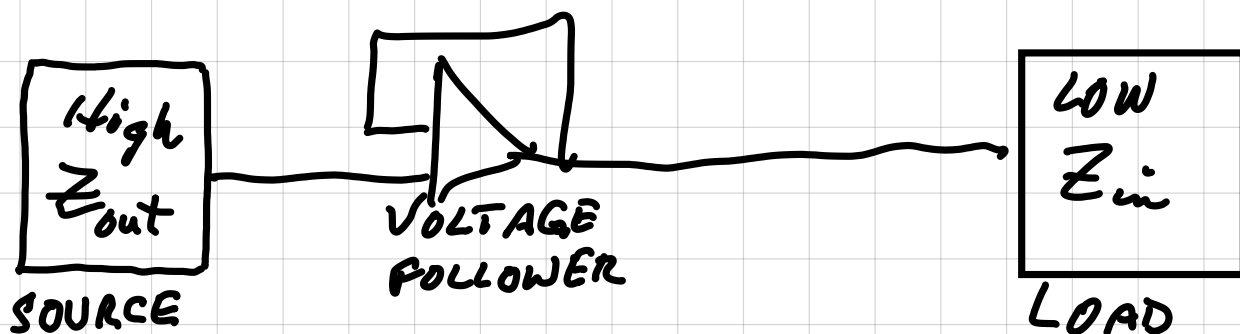Voltage follower ckt.  
(Has high  $Z_{in}$  and low  $Z_{out}$ )



Isolates load from source.  
(without voltage follower, load would see very little voltage from source)