

EE3 Fall 2020

Homework Problem 2

Find the current through the battery, two ways:

- with V_4 as the reference node
- with V_2 as the reference node

