

EE3 Fall 2020

Homework Problem 3

The switch has been in position a for a long time. At $t=0$, it moves instantaneously to position b. Find:

- a. $v_c(0^-)$
- b. $v_c(0^+)$
- c. $i_o(0^-)$
- d. $i_o(0^+)$
- e. [EXTRA CREDIT] $v_c(t)$

