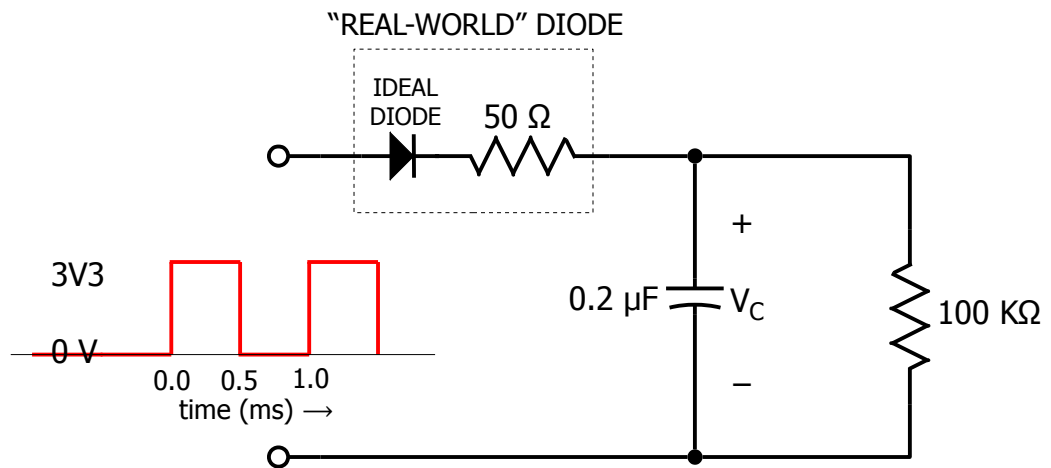


EE3 Fall 2020

Homework Problem 4



The input voltage has been at 0 V for a long time. All transients have died out. At time $t = 0.0$, a 3V3 pulse train begins. NOTE: the device inside the dashed-line box is an approximation of a real-world diode: when the left end is positive with respect to the right end, it is **forward-biased** and its resistance is $50\ \Omega$. When the left end is negative, it is **reverse-biased** and its resistance is ∞ .

- When the input voltage is 3V3, the diode is forward-biased; $3\text{V3} > v_C$. What is the charging time constant? Neglect the effect of the $100\ \text{k}\Omega$ resistor.
- When the input voltage is 0 V, the diode is reverse-biased, $v_C > 0\ \text{V}$, and the capacitor can discharge only through the $100\ \text{k}\Omega$ resistor. What is the discharging time constant?
- What is v_C at time 0.0^+ ?
- What is v_C at time 0.5^+ ? You will need to evaluate the equation describing the behavior as shown on Slide 3 of Lecture 4 on CCLE Week 3.
- What is v_C at time 1.0^+ ? Remember that v_C cannot change in the transition from 0^- to 0^+ .
- Based on what you see in (d.) and (e.), predict the value of v_C at time 1.5^+ .

$$\text{a. } \tau_{chg} = (50) \cdot (0.2\text{e-}6) = 10\ \mu\text{s}$$

$$\text{b. } \tau_{dischg} = (100\text{e}3) \cdot (0.2\text{e-}6) = 20\ \text{ms}$$

$$\text{c. } v_C(0^+) = v_C(0^-) = 0\ \text{V}$$

$$\text{d. } v_C(0.5\text{e-}3^+) = v_C(0.5\text{e-}3^-) = 3.3 \cdot \left(1 - e^{\frac{-0.5\text{e-}3}{50 \cdot 0.2\text{e-}6}}\right) \approx 3.3 \cdot (1 - 0) = 3.3\ \text{V}$$

$$\text{e. } v_C(1.0\text{e-}3^+) = v_C(1.0\text{e-}3^-) = 3.3 \cdot e^{\frac{0.5\text{e-}3}{100\text{e}3 \cdot 0.2\text{e-}6}} = 3.3 \cdot e^{-0.025} = 3.22\ \text{V}$$

$$\text{f. Prediction: } v_C = 3.3\ \text{V}$$