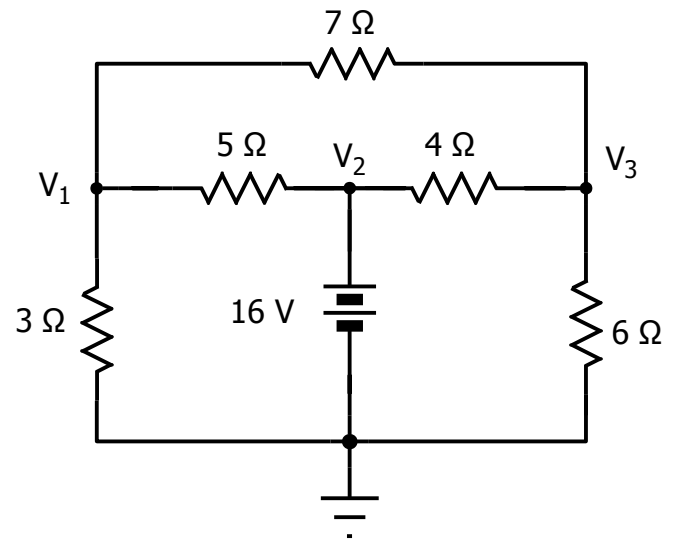


## EE3 Fall 2020 Practice Problems 5

1. More NVA practice. Find  $V_1$  &  $V_3$ .




$$V_1 = 6.6 \text{ V}; V_3 = 8.83 \text{ V}$$

## EE3 Fall 2020

### Practice Problems 5

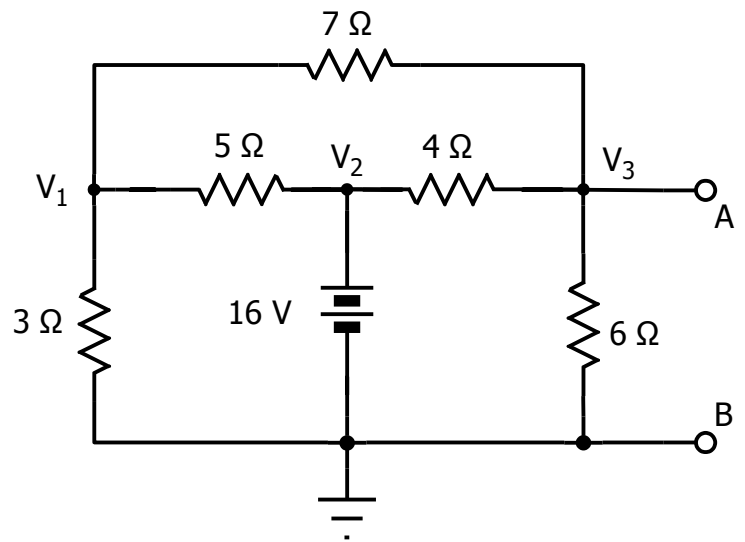2. In this circuit,  $V_3 = 8.8 \text{ V}$ . You will be using Method (a.) to find the Thévenin Equivalent circuit.

Use the  $V_{OC}$ - $I_{SC}$  method to find the Thévenin Equivalent circuit, looking in through Port A-B.




$$R_{th} = 1.88 \, \Omega$$

## EE3 Fall 2020

### Practice Problems 5

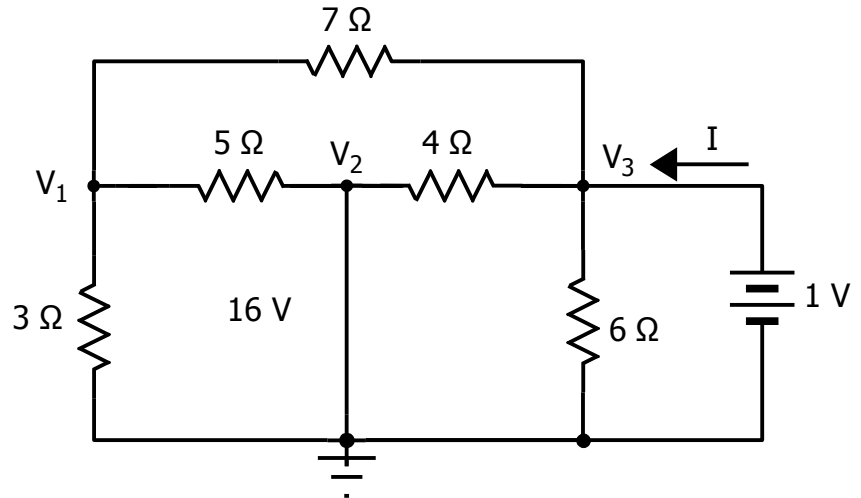3. This time, you will find the Thévenin Equivalent circuit by using Method (b.). We zeroed out the 16 V battery and attached a test battery to the circuit as shown.
- Find an expression for the current  $I_T$ .
  - Compute  $V_T / I_T$ . Units are ohms.
  - Compare your answer to Problem 2.




$$R_{th} = 1.89 \, \Omega$$

## EE3 Fall 2020


### Practice Problems 5

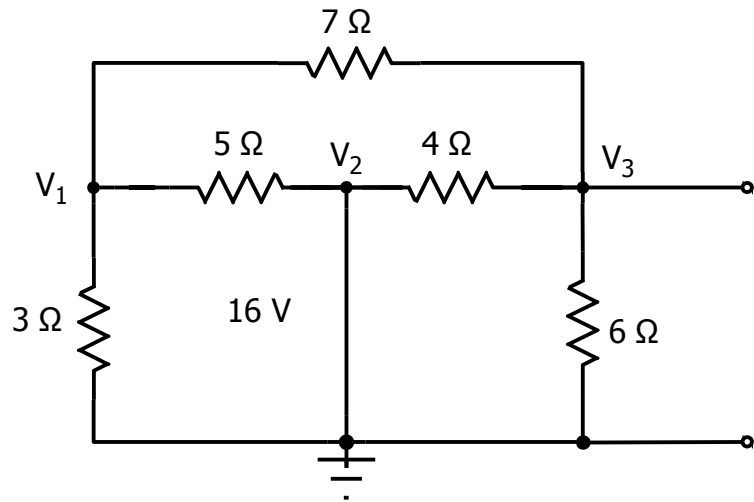4. This time, you will find the Thévenin Equivalent circuit by using Method (c.). We replaced the 16 V battery with a short.
- Using your knowledge of series and parallel circuits, find the resistance of the circuit when looking in through the port.
  - Compare your answer to Problem 3.


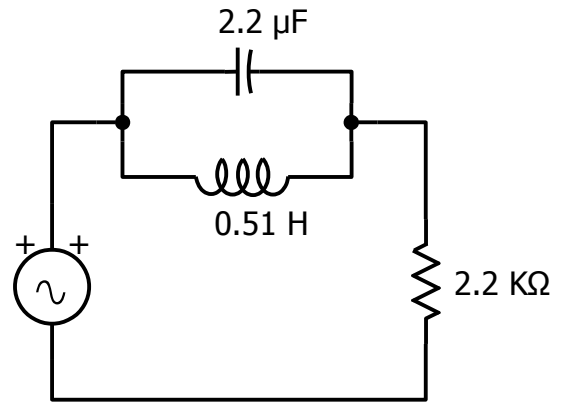
## EE3 Fall 2020 Practice Problems 5

- 5a. Using the expressions for capacitive and inductive impedance, find the total impedance presented by the capacitor, inductor, and resistor to the voltage source. Set  $\omega = 1000$  rad/s.



$$Z_{tot} = 2200 - j4180$$

- b. Now find the current through the voltage source if  $v(t) = 10 \cos(1000t)$ . Express in both rectangular and polar forms.

$$i_V(t) = 0.99 + j1.87 \text{ mA} = 2.12 \angle 62.1^\circ$$

- d. Find the current through the inductor  $i_L$ . Express in both rectangular and polar forms.

$$i_L(t) = -8.1 - j15.4 \text{ mA} = 17.4 \angle -118^\circ$$

- e. Find the current through the capacitor  $i_C$ .

$$i_C(t) = 9.1 + j17.2 \text{ mA}$$

- f. Add  $i_L$  and  $i_C$ . The sum should equal the current in #2.

$$i_L + i_C = 0.99 + j1.87 \text{ mA}$$

- g. Compare the magnitudes of  $i_L(t)$ ,  $i_C(t)$ , and  $i_V(t)$ . Can you explain the apparent anomaly?