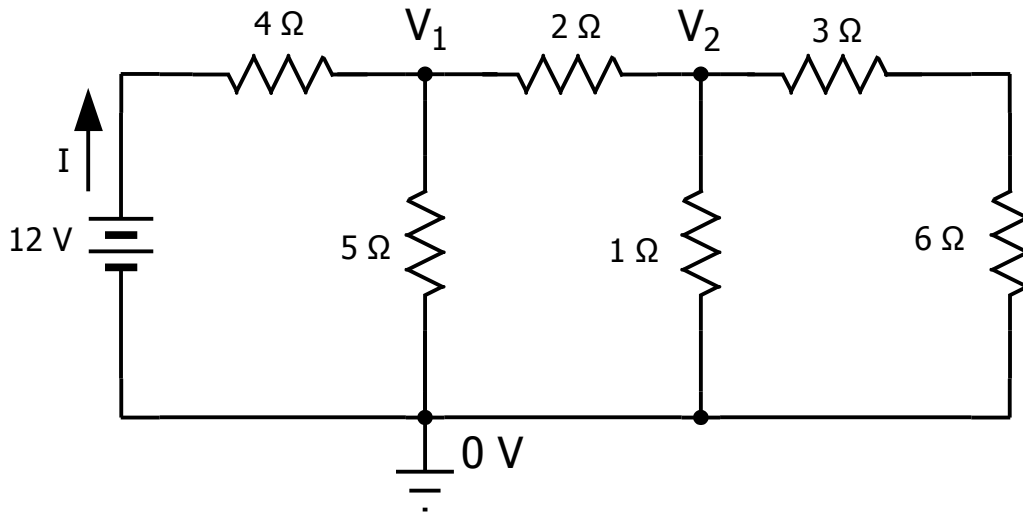


## EE3 Fall 2020

### Homework Problem 1



1. Watch and study the KVL-KCL video as posted under Week 1.
  - a. Assuming that all of the currents at Node 1 (where  $V_1$  is) are \*leaving\* the node, write an Ohm's Law expression for the current going through the  $4\ \Omega$  resistor.
  - b. Under the same assumption, write an Ohm's Law expression for the current through the  $5\ \Omega$  resistor.
  - c. Continuing, write an expression for the current through the  $2\ \Omega$  resistor.
  - d. Now, combine the answers to 1a,b,c into a KCL equation.
  - e. Now, following the procedures in a, b, and c, write Ohm's Law expressions for the three currents leaving Node 2.
  - f. Combine the three answers to 1e into a second KCL equation.
2. You now have 2 equations in 2 unknowns. Solve them for  $V_1$  and  $V_2$ .
3. Now that you know  $V_1$ , you can compute  $I$ .