

## EE3 Fall 2020 Practice Problems 7

1. Compute the forward resistance of the 1N4448 diode when working in the normal operating range of 4-20 mA.


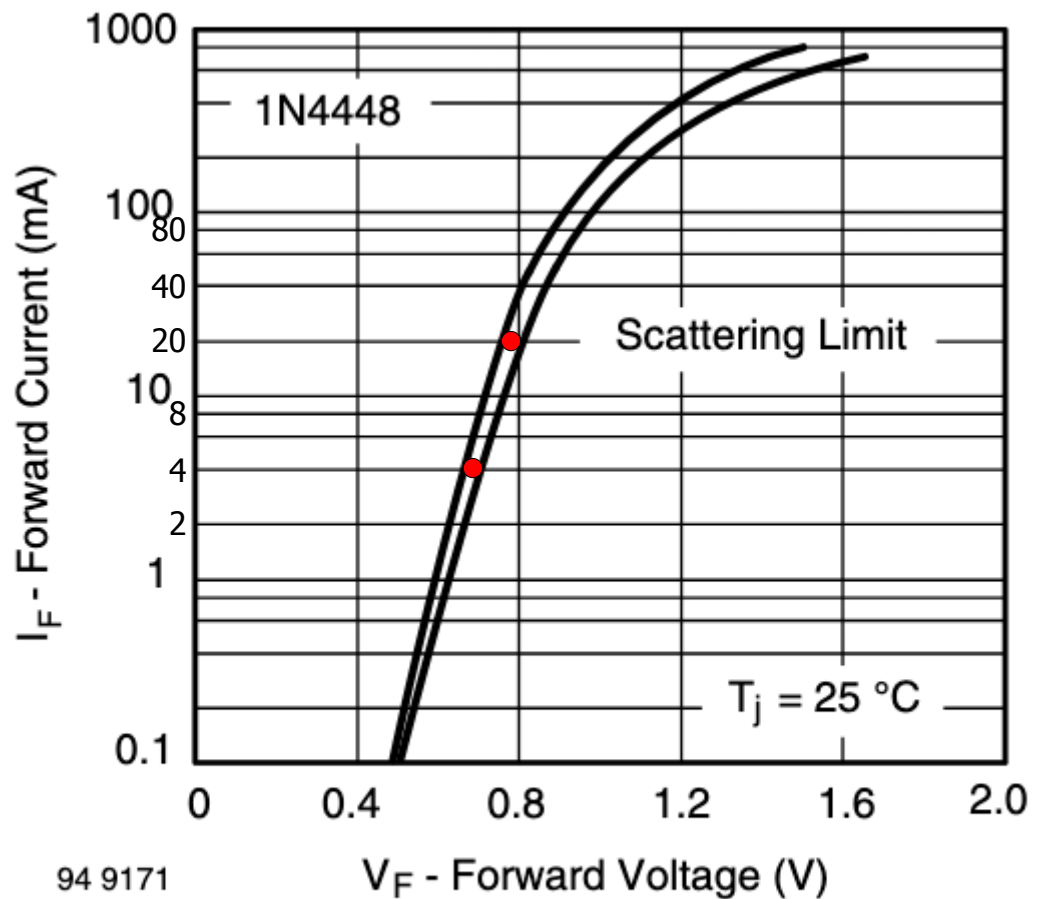
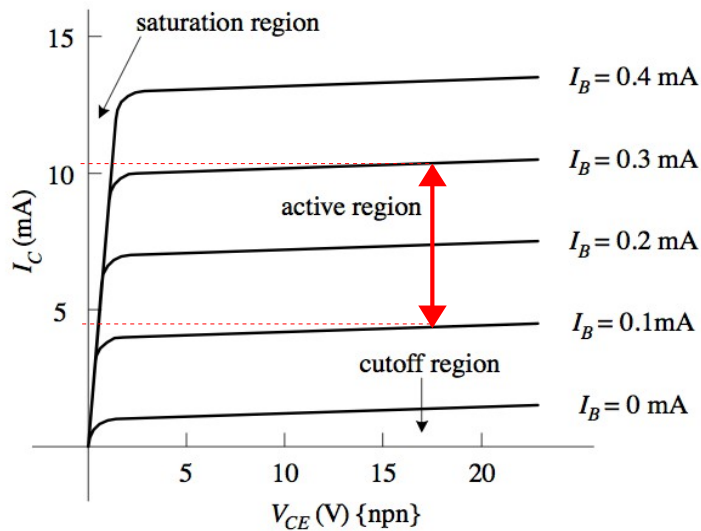


Fig. 2 - Forward Current vs. Forward Voltage

$$R = \frac{(0.8 - 0.7)\text{ V}}{(20 - 4)\text{ mA}} = 6.25\text{ }\Omega$$

## EE3 Fall 2020 Practice Problems 7

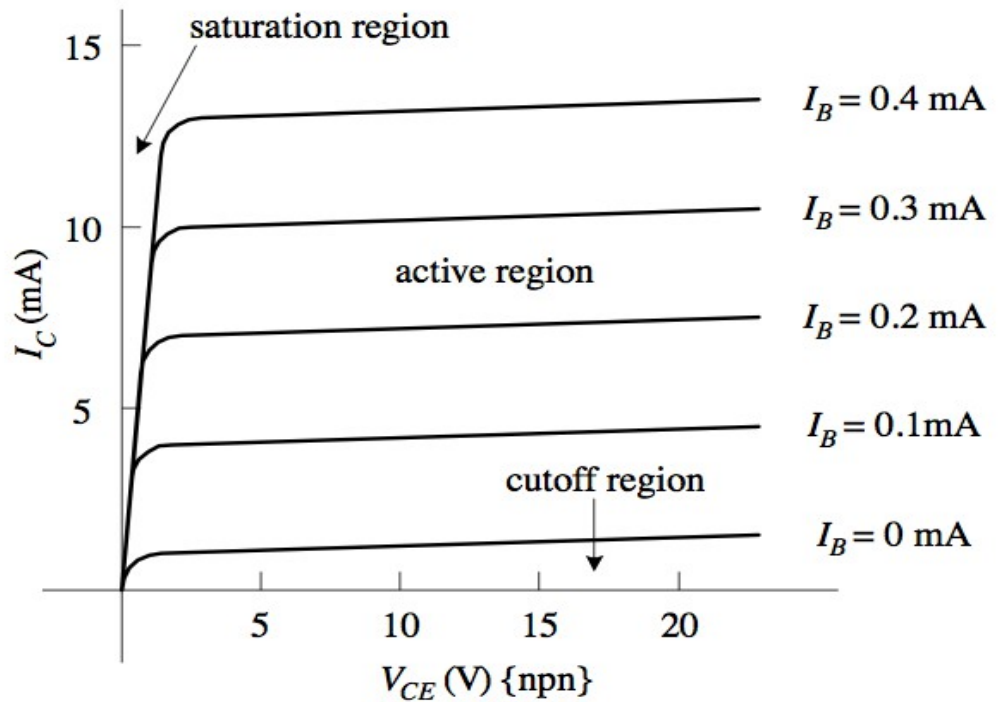
2. Compute the approximate current gain of this NPN transistor if the input base current is  $\pm 0.1$  mA with an offset of 0.2 mA. Current gain  $G = I_C/I_B$ .



$$G = \frac{\Delta I_C}{\Delta I_B} = \frac{(10 - 4) \text{ e-3}}{(0.3 - 0.1) \text{ e-3}} = \frac{6 \text{ e-3}}{0.2 \text{ e-3}} = 30 \text{ (rather low for a BJT)}$$

## EE3 Fall 2020 Practice Problems 7

One can make use of resonance to provide amplification at a given frequency. In this circuit, we want the gain  $|V_{out}/V_{in}|$  to be 10 at 1 KHz. Find L and C.

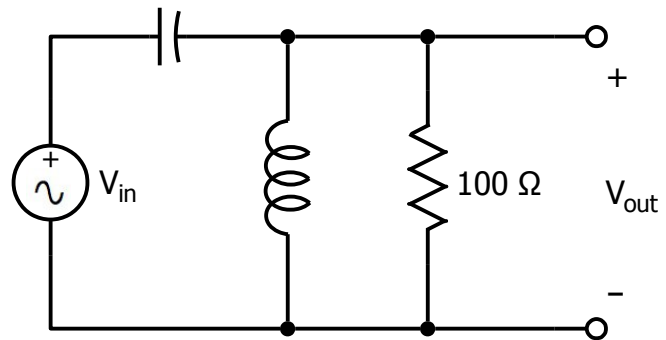

$$\frac{V_{out}}{V_{in}} = \frac{R \parallel Z_L}{Z_C + R \parallel Z_L} = \frac{\frac{j\omega RL}{R + j\omega L}}{\frac{1}{j\omega C} + \frac{j\omega RL}{R + j\omega L}} = \frac{j\omega L}{j\omega L + \frac{j\omega L + R}{j\omega RC}} = \frac{j\omega L}{j\left(\omega L - \frac{1}{\omega C}\right) + \frac{L}{RC}}$$

Gain is max at resonance when  $\omega L = \frac{1}{\omega C}$

$$\left| \frac{V_{out}}{V_{in}} \right| = 10 = |j\omega RC| = 2\pi(100) \cdot (1000) C \rightarrow C = 15.9 \mu\text{F}$$

$$L = \frac{1}{\omega^2 C} = 1.59 \text{ mH}$$