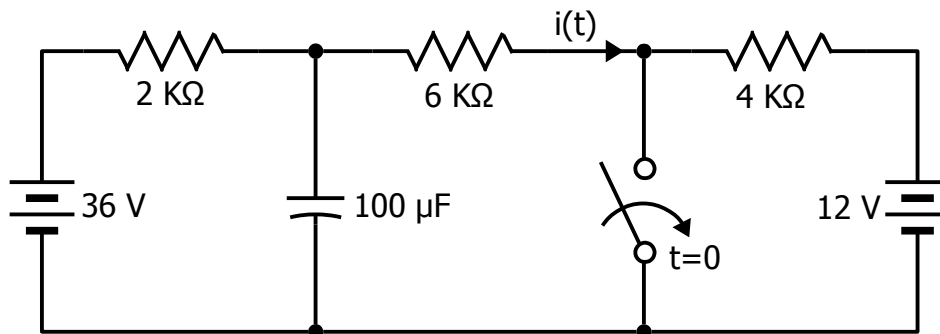


EE3 Fall 2020

Homework Problem 7

This problem is all about $i(t)$.


- What is $i(0^-)$?
- What is $i(0^+)$?
- What is $i(\infty)$?
- What is $i(t)$, $t > 0$?



The circuit has been in this condition for a long time.


This problem can be solved without using a differential equation, though you may do so this way if you wish. Solving it without using a differential equation is done by pulling together a few ideas and bringing them to bear on the problem. That means using the answers to the first 3 parts of this problem, plus the judicious use of a Thévenin equivalent, plus the third slide of Lecture 4 in Week 4 of CCLE.

Thévenin Equivalent Solution:

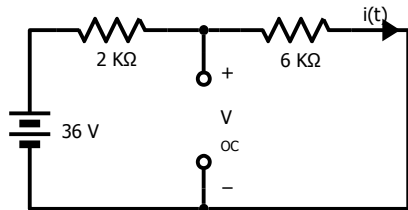

$$V_{th} = V_{OC} = (36) \left(\frac{6}{6+2} \right) = 27 \text{ V}$$
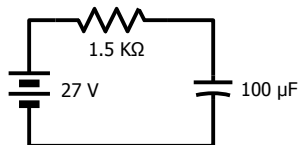
$$R_{th} = 2\text{e}3 \parallel 6\text{e}3 = 1.5 \text{ K}\Omega$$



$$v_C(0^+) = v_C(0^-) = 12 + (36 - 12) \cdot \left(\frac{(6\text{e}3 + 4\text{e}3)}{(6\text{e}3 + 4\text{e}3) + 2\text{e}3} \right) = 32 \text{ V}$$

By Lecture 4, third slide, $v_C(t) = V_S - [V_S - v_C(0^+)] e^{-\frac{t}{RC}}$

$$v_C(t) = 27 - [27 - 32] e^{-\frac{t}{(1.5\text{e}3)(100\text{e-}6)}} = 27 + 5 e^{-\frac{t}{0.15}}$$

$$i(t) = \frac{v(t)}{6\text{e}3} = (4.5 + 0.83 e^{-\frac{t}{0.15}}) \text{ mA}$$

ODE Solution:

$$\frac{v-36}{2\text{e}3} + C \frac{dv_C}{dt} + \frac{v}{6\text{e}3} = 0$$

$$\frac{dv_C}{dt} + 6.67 v_C = 180$$

$$P = 6.67; Q = 180 \rightarrow \int_0^t P dX = e^{6.67t}$$

$$e^{6.67t} \frac{dv_C}{dt} + 6.67 e^{6.67t} v_C = e^{6.67t} 180$$

$$\frac{d}{dt} (e^{6.67t} v_C) = 180 e^{6.67t}$$

$$e^{6.67t} v_C = 100 \int e^{6.67t} dt = 27 e^{6.67t} + C$$

$$v_C(t) = 27 + C e^{-6.67t}$$

$$v_C(0^+) = 32 = 27 + C \rightarrow C = 5$$

$$v_C(t) = 5 e^{-6.67t} + 27$$

$$i(t) = 0.83 e^{-6.67t} + 4.5$$